

2018  
MCA  
MCA : 1.2  
DIGITAL SYSTEM

Full Marks: 75

Time : 3 hours

*The figures in the margin indicates full marks for the questions*

1. Fill in the blanks: 5X1=5
  - I.  $457_8 = \dots\dots\dots)_2$
  - II. The base of Decimal number is .....
  - III. 1 byte = ..... bits
  - IV. A Filp-Flop has ..... unit of memory
  - V. Race Around condition is the disadvantage of ..... Filp-Flop
2. Find  $(-14)_{10} = \dots)_2$ , by following all the negative number representation techniques of Binary number system. 9
3. Differentiate between : 5X2=10
  - a. Sequential Circuit & Combinational Circuit
  - b. Synchronous Circuit & Asynchronous Circuit
4. Design a Half Adder and a Full Adder, and study their I/O characteristics. 4+6=10
5. Design a (8:1) Multiplexer 7
6. State and Prove the DeMorgan's Theorem. 2+2+3+3=10
7. What are the functional characteristics of Decoder? Design a (3:8) encoder. 5+5=10
8. Write short notes on : (Any Two) 2 × 7=14
  - a. R-S Filp-Flop
  - b. Race Around Condition
  - c. Subtractor

\*\*\*\*\*