

**2023**

**INFORMATION TECHNOLOGY**

**Paper : ITBHC3056**

**( Digital Logic and ICT )**

Full Marks : 60

Pass Marks : 24

**Time : 3 hours**

*The figures in the margin indicate full marks  
for the questions*

**1. Choose the correct answer (any five) : 1×5=5**

(a) A register capable of incrementing and/or decrementing its contents is termed as

(i) counter

(ii) decoder

(iii) multiplexer

(iv) demultiplexer

(b) In Boolean algebra  $(A \cdot \bar{A}) + A = ?$

(i) 0

(ii) A

(iii)  $\bar{A}$

(iv) 1

(c) D flip-flop can be made from a J-K flip-flop by making which of the following conditions?

- (i)  $J = K$
- (ii)  $J = K = 1$
- (iii)  $J = 0, K = 1$
- (iv)  $J = \bar{K}$

(d) How many entries will be in the truth table of a 5-input NAND gate?

- (i) 6
- (ii) 8
- (iii) 32
- (iv) 16

(e) In the toggle mode, a J-K flip-flop has

- (i)  $J = 0, K = 1$
- (ii)  $J = 1, K = 1$
- (iii)  $J = 0, K = 0$
- (iv)  $J = 1, K = 0$

(f) The total amount of memory depends upon

- (i) the organization of memory
- (ii) the size of decoding unit
- (iii) the size of the address bus of microprocessor
- (iv) the structure of memory

(g) Which memory uses the concept of tracks and sectors?

- (i) SRAM
- (ii) Hard disk
- (iii) DRAM
- (iv) Magnetic tape

(h) Which memory cannot be accessed directly by the CPU of the computer?

- (i) RAM
- (ii) Cache memory
- (iii) ROM
- (iv) Memory card

(i) Which of the following is used in main memory?

- (i) DRAM
- (ii) DDR
- (iii) SRAM
- (iv) PRAM

(j) Which of the following is the fastest memory?

- (i) Hard Disk
- (ii) DVD ROMs
- (iii) Static RAM
- (iv) Cache Memory

( 4 )

2. Answer the following questions (any five) :  
2×5=10

- (a) State and prove De Morgan's law.
- (b) What is modern computer?
- (c) Differentiate between adder and subtractor.
- (d) What do you mean by flip-flop? Write any two uses of flip-flop.
- (e) List any four names of intel processor family.
- (f) What is CD-ROM?
- (g) What do you mean by defragmentation?

3. Answer the following questions (any five) :  
5×5=25

- (a) Simplify the Boolean function to the required number of literals :  $2\frac{1}{2}+2\frac{1}{2}=5$ 
  - (i)  $AB + AB'C + BC'$
  - (ii)  $(X + XY)(X + X'Y)(X + Z)$
- (b) What is PLA? Implement the following function using PLA :  $1+4=5$   
 $F_1 = \Sigma_m(3, 5, 7)$   
 $F_2 = \Sigma_m(4, 5, 7)$
- (c) State five differences between cache memory and virtual memory. 5

( 5 )

(d) Explain the following terms :  $2\frac{1}{2}+2\frac{1}{2}=5$

- (i) Keyboard
- (ii) Speaker

(e) What do you mean by minterm and maxterm? Find out the minterm and maxterm expressions for the following equation :  $2+3=5$

$$Y = \Sigma(5, 6, 7, 9, 11, 12)$$

(f) Define RAM. Explain the different kinds of RAM.  $1+4=5$

(g) Design (8 : 1) multiplexer. Draw its logic diagram. 5

(h) Explain the following terms :  $2\frac{1}{2}+2\frac{1}{2}=5$

- (i) CD
- (ii) DVD

(i) Write any five applications of demux. 5

4. Answer the following questions (any two) :  
 $10 \times 2 = 20$

- (a) What is J-K flip-flop? Find out the characteristic equation of J-K flip-flop using characteristic table. How is D flip-flop different from J-K flip-flop? Write any three applications of J-K flip-flop.  $1+3+3+3=10$

- (b) (i) What do you mean by Karnaugh map? Simplify the following expression using K-map : 5

$$Y = (0, 1, 3, 5, 7, 8, 9, 10, 11)$$

- (ii) What is logic gates? Explain different type of logic gates using truth table. 5

- (c) Define motherboard. What are the different types of motherboard? Explain. 10

- (d) (i) Write the differences between edge triggering and level triggering.

- (ii) Explain FAT and NTFS file system.

- (iii) Explain decoder using truth table.

$$3+4+3=10$$

\*\*\*