

63/1 (SEM-3) CC7/PHYHC3076

2023

PHYSICS

Paper : PHYHC3076

(Digital Systems and Applications)

Full Marks : 60

Pass Marks : 24

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer (any five) : 1×5=5

(a) The input impedance of CRO is

- (i) around one ohm**
- (ii) around one mega ohm**
- (iii) around one kilo ohm**
- (iv) around one giga ohm**

**(b) It is not possible to produce ICs of
power rating more than**

- (i) 1 watt**
- (ii) 10 watt**
- (iii) 100 watt**
- (iv) 1000 watt**

(2)

- (c) The number system which uses alphabets as well as numerals to represent its digits is
- (i) octal
 - (ii) decimal
 - (iii) alphanumeric code
 - (iv) hexadecimal
- (d) The logic gate that provides high outputs for same inputs is
- (i) NOR
 - (ii) NAND
 - (iii) XOR
 - (iv) XNOR
- (e) In which operation carry is obtained?
- (i) Subtraction
 - (ii) Addition
 - (iii) Multiplication
 - (iv) Both addition and subtraction
- (f) How many select lines would be required for an 8-line to 1-line multiplexer?
- (i) 2
 - (ii) 3
 - (iii) 8
 - (iv) 1

(3)

- (g) What does the bubble at the left of a triangle on the clock of a flip-flop mean?
- (i) Level triggered
 - (ii) Edge triggered
 - (iii) Positive edge triggered
 - (iv) Negative edge triggered
- (h) Astable mode is also called
- (i) bounded
 - (ii) free running
 - (iii) neutral
 - (iv) single
- (i) The type of register used to construct a ring counter is
- (i) SISO
 - (ii) SIPO
 - (iii) PISO
 - (iv) PIPO
- (j) Ripple counters are called
- (i) SSI counters
 - (ii) asynchronous counters
 - (iii) synchronous counters
 - (iv) VLSI counters

(4)

2. Answer any *five* of the following questions :

2×5=10

- (a) What are the advantages of CRO in comparison to multimeter?
- (b) List out at least two disadvantages of IC.
- (c) Convert the following hexadecimal numbers to decimal numbers : 1+1=2
 - (i) $(FE7)_{16}$
 - (ii) $(3C.2A)_{16}$
- (d) What do you mean by duality principle in Boolean algebra?
- (e) What do you mean by an encoder? What are its different types? 1+1=2
- (f) What is a race around condition? How can it be corrected? 1+1=2
- (g) Define 'Opcode' and 'Operand'. 1+1=2

3. Answer any *five* of the following questions :

5×5=25

- (a) Realize with figures 2-input AND gate both for diodes and transistors, also draw the truth table of it. 2+2+1=5
- (b) What is de-multiplexer? Draw the circuit of 1-4 de-multiplexer, explain its working with truth table. 1+1+2+1=5
- (c) Write in brief about computer memory mentioning its different types.

24KB/138

(Continued)

(5)

- (d) What are the different software tools for assembly language programming? Write in brief about them.

2+3=5

- (e) What do you mean by R-S flip-flop? Realize R-S flip-flop with NOR gates and describe its different input conditions.

1+2+2=5

- (f) What is an adder? Draw the full-adder circuit and show its detail input and output with appropriate truth-table.

1+2+2=5

- (g) Convert the following Boolean function into standard sum of products and express it in terms of minterms :

$$Y(A, B, C) = AB + A\bar{C} + BC \quad 2\frac{1}{2}+2\frac{1}{2}=5$$

- (h) What is a decade counter? Draw its circuit. Write its truth-table mentioning its working.

1+2+2=5

- (i) What are different types of measurement of phase difference by a CRO? Explain any one of them. What is the difference between CRO and a DSO?

1+3+1=5

4. Answer any *two* of the following questions :

10×2=20

- (a) Draw the neat block diagram of 8085 microprocessor. Explain its different components.

5+5=10

24KB/138

(Turn Over)

(6)

- (b) Describe a monostable multivibrator using IC555 timer with necessary circuit diagram. What is time delay? A monostable multivibrator has $R = 120\text{ K}$ and the time delay $T = 1000\text{ ms}$, calculate the value of C. $6+2+2=10$
- (c) What is a K-map? Write in detail how will you roll out a K-map from the following 2-variable and 3-variable truth-tables. $2+3+5=10$

(i)

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1

(ii)

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(7)

- (d) Write short notes on the following : $5 \times 2 = 10$
- (i) Integrated circuit
- (ii) Theorems of Boolean algebra with examples
